



Computer Architecture HW2:

Simple ALU Unit

TA: Ting Wang (王珽)

Email: d10943014@ntu.edu.tw



Goal


- ◆ Implement an unsigned multiplier
- ◆ Implement an unsigned divider
- ◆ Implement SHIFT operation
- ◆ Implement AVG operation
- ◆ Combine the 4 operations into single unit (ALU)

- ◆ In this homework, you will learn:
 - ◆ How to use assignments with `wire`
 - ◆ How to use always blocks with `reg`
 - ◆ How to describe combinational and sequential circuits
 - ◆ How to control state machine
 - ◆ How to develop a good coding style



Quick Review: Multiplication Circuit

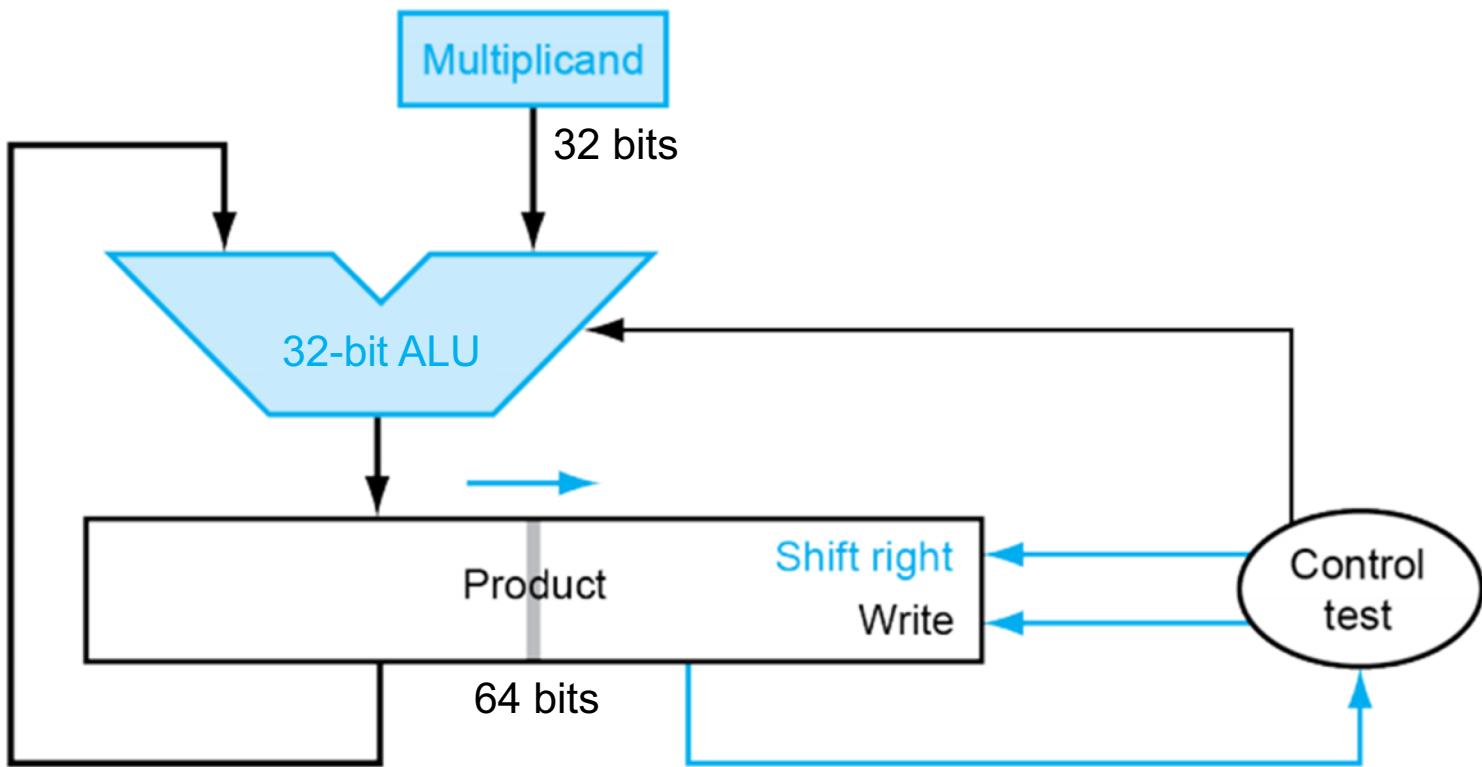
- ◆ Reduced register consumption
- ◆ Reduced size of ALU





Quick Review: Division Circuit

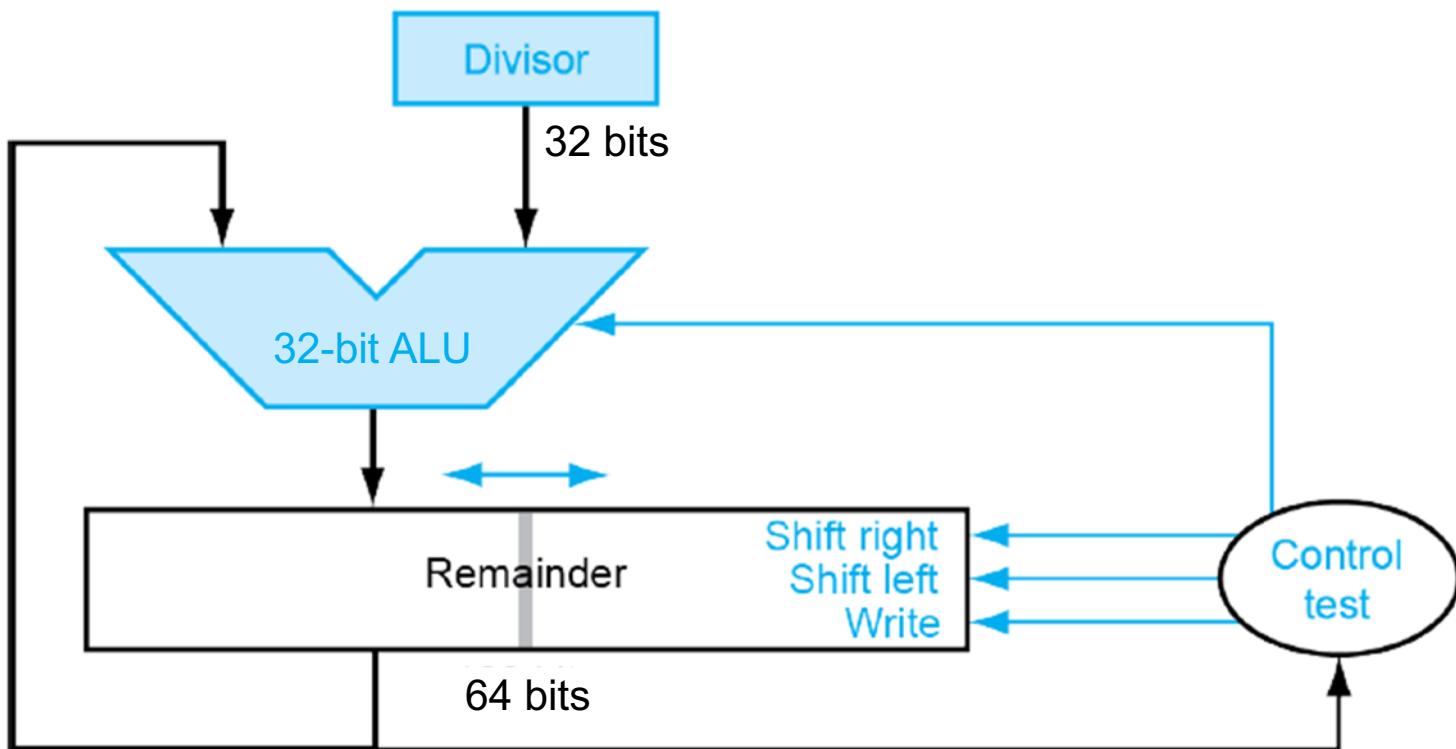
- ◆ Reduced register consumption
- ◆ Reduced size of ALU





Observation

 
- ◆ The structures of both multiplier and divider are similar
 - ◆ Operand register
 - ◆ ALU
 - ◆ Shift register
- ◆ Reuse the hardware!






AND/AVG Operation

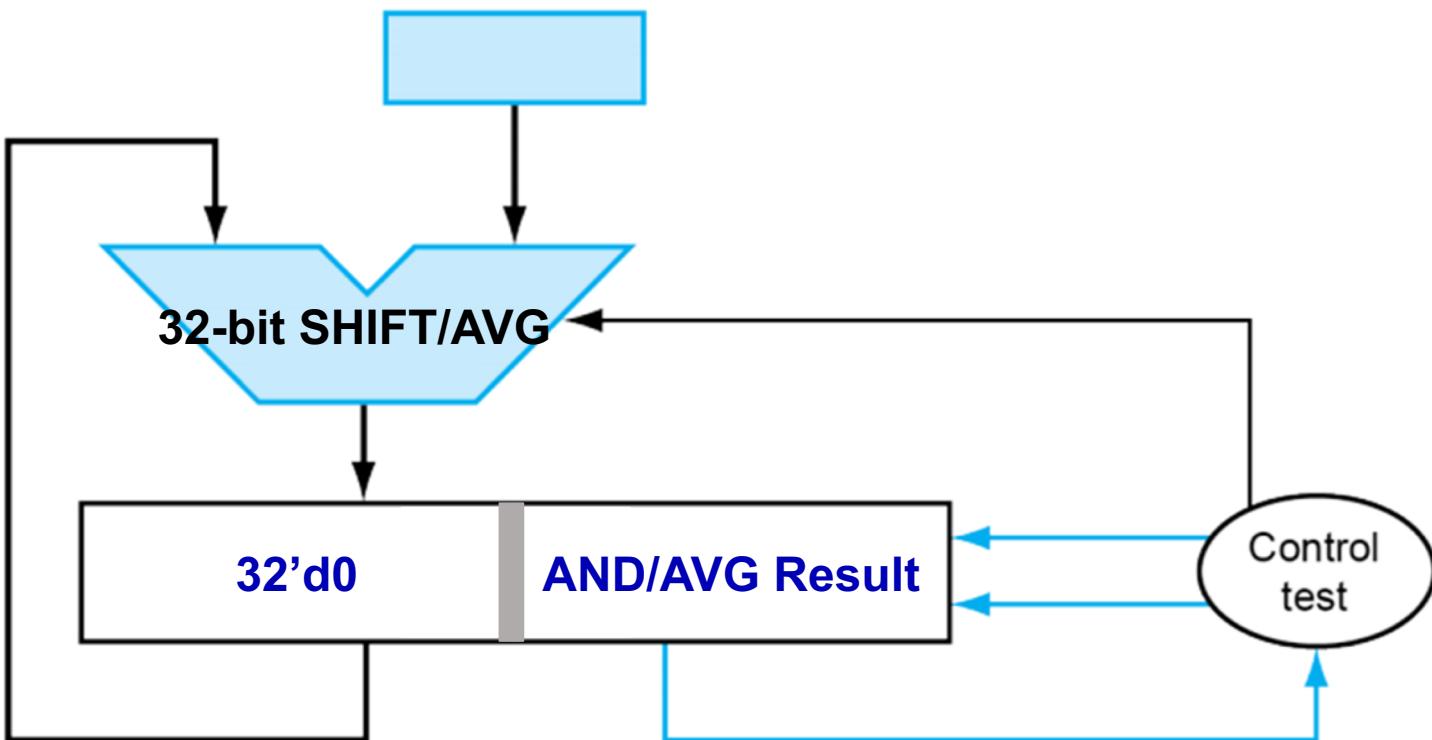- ◆ 32-bit ALU can also perform SHIFT/AVG Operation
- ◆ The most significant 32 bits of Remainder register should remain 32'd0
- ◆ Share the hardware with multiplication/division





Specification

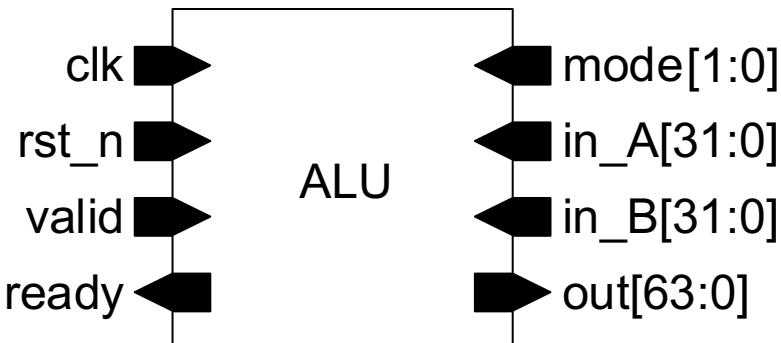

Name	I/O	Width	Description
clk	I	1	Positive edge-triggered clock
rst_n	I	1	Asynchronous negative edge reset
valid	I	1	Valid input data when valid = 1
ready	O	1	Ready output data when ready = 1
mode[1:0]	I	2	0: multiplication, 1: division 2: SHIFT, 3: AVG
in_A[31:0]	I	32	Input A
in_B[31:0]	I	32	Input B
out[63:0]	O	64	Output



Specification

- ◆ Multiplication
 - ◆ Unsigned input (32b)
 - ◆ $\text{out} = \text{in_A} \times \text{in_B}$ (32b \times 32b \rightarrow 64b)
- ◆ Division
 - ◆ Unsigned input (32b)
 - ◆ $\text{quotient} = \text{in_A} / \text{in_B}$ (quotient is 32b)
 - ◆ $\text{remainder} = \text{in_A \% in_B}$ (remainder is 32b)
 - ◆ $\text{out} = \{\text{remainder}, \text{quotient}\}$
- ◆ SHIFT 看這邊的二進位數字代表多少，A就要右移幾位
 - ◆ in_A will be right shifted by $\text{in_B}[2:0]$ bits
 - ◆ $\text{out} = \{32'd0, \text{shift result}\}$
- ◆ AVG
 - ◆ $\text{out} = \text{average of in_A and in_B}$ (round down to integer)




Design Issues

- ◆ Require 1 cycle to load data
 - ◆ Require 32 cycles to do multiplication/division
 - ◆ Require 1 cycle to do SHIFT/AVG
 - ◆ Require 1 cycle to output data
-
- ◆ Consider CPU is issuing a task to ALU
 - ◆ Valid input to ALU for only 1 cycle
 - ◆ Expect to receive ready output from multiplication/division after 32 cycles
 - ◆ Expect to receive ready output from SHIFT/AVG after 1 cycle



Waveform

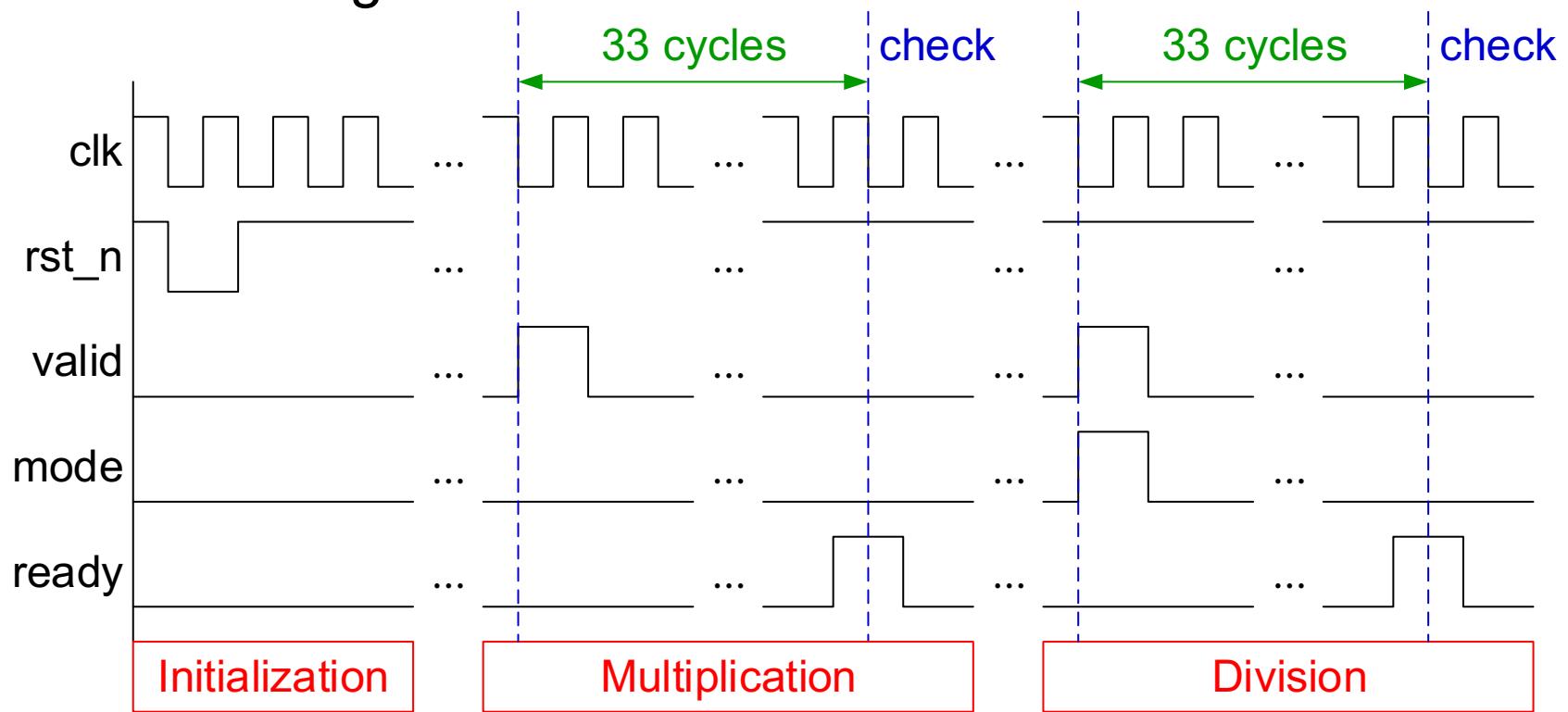
- ◆ The testbench checks the result after 33 cycles once valid changes to 1 for multiplication/division
- ◆ The testbench checks the result after 2 cycles once valid changes to 1 for SHIFT/AVG





Finite State Machine (FSM)

- ◆ Requires a counter to record the process

 



Todo 1: FSM

- ◆ Define your finite state machine
- ◆ Notice the syntax

```
parameter IDLE = 3'd0;
parameter MUL = 3'd1;
parameter DIV = 3'd2;
parameter SHIFT = 3'd3;
parameter AVG = 3'd4;
parameter OUT = 3'd5;
```

```
always @(*) begin
    case(state)
        IDLE: begin
            ...
        end
        MUL :
        DIV :
        SHIFT :
        AVG :
        OUT : state_nxt = IDLE;
        default :
    endcase
end
```

```
// Todo: Sequential always block
always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        state <= IDLE;
    end
    else begin
        state <= state_nxt;
    end
end
```



Todo 2: Counter


- ◆ Hint
 - ◆ Counter counts from 0 to 31 when the state is MUL or DIV
 - ◆ Otherwise, keep it zero

- ◆ Please describe it with Verilog



Operand Register (alu_in)

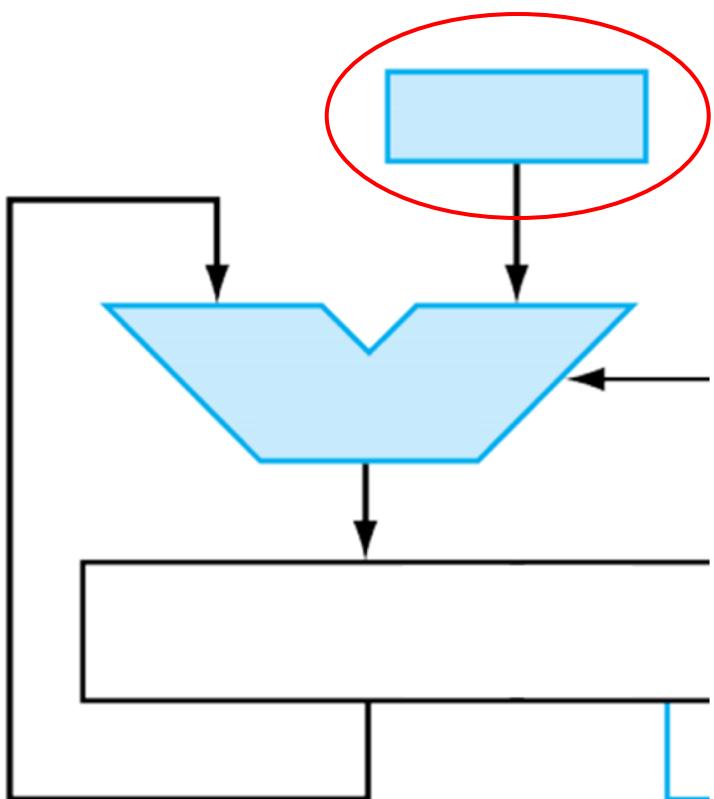- ◆ Load data when the state is IDLE and valid = 1
- ◆ When the state is back to IDLE, clear it




```
// ALU input
always @(*) begin
    case(state)
        IDLE: begin
            if (valid) alu_in_nxt = in_B;
            else         alu_in_nxt = 0;
        end
        OUT : alu_in_nxt = 0;
        default: alu_in_nxt = alu_in;
    endcase
end
```



Todo 3: ALU


- ◆ Multiplication: addition / Division: subtraction
- ◆ SHIFT/AVG operation
- ◆ You should consider
 - ◆ Bit width of ALU (to handle overflow)
 - ◆ Which bit range of shift register should be transmitted to ALU
 - ◆ The operation in ALU given current state

 



Todo 4: Shift Register


- ◆ Load data to the low 32 bits when the state is IDLE and valid = 1
- ◆ Multiplication: update data and **right shift**
- ◆ Division: update data and **left shift**

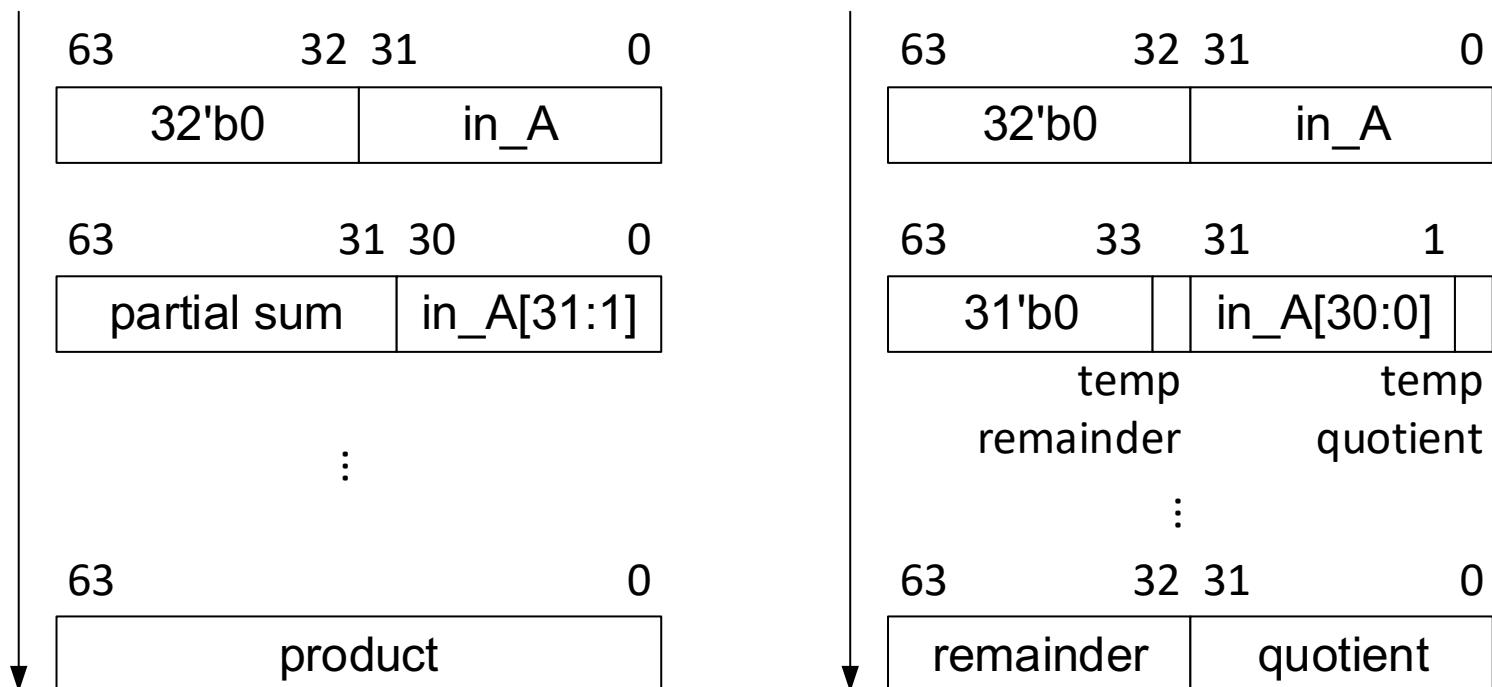



Todo 4: Shift Register (Cont.)

- ◆ Load data to the low 32 bits when the state is IDLE and valid = 1
- ◆ SHIFT: update data
- ◆ AVG: update data

 



Todo 5: Output Control

- ◆ Relate output port “out” to shift register
- ◆ When is your circuit “ready” to output?

- ◆ For such simple description, one can use wire assignments
 - ◆ Hint: output is default wire-typed



Simulation

- ◆ There are two files in folder named “code”
 - ◆ HW2.v (homework)
 - ◆ HW2_tb.v (testbench)
- ◆ To run simulation, you should run source command in advance
 - ◆ \$ source license.cshrc (use given file)
- ◆ Verilog simulation
 - ◆ \$ ncverilog HW2_tb.v HW2.v +access+r



Modify the Testbench

- ◆ The testbench will run `NUM_DATA multiplications and `NUM_DATA divisions
- ◆ Between the time checking the result and the new valid input, there will be at most `MAX_DELAY cycles

```
// You can modify NUM_DATA and MAX_DELAY
`define NUM_DATA 10
`define MAX_DELAY 3
```

- ◆ Change input to what you want
 - ◆ Example: multiplication

```
// Multiplication
$display("-----");
$display("Test function of multiplication...");
for (i=1; i<`NUM_DATA; i=i+1) begin
    delay_num = $abs($random()%`MAX_DELAY)+1;
    #(`CLCYE_TIME*delay_num)
    valid = 1;
    A = $random()%32'hFFFF_FFFF; // change your pattern here
    B = $random()%32'hFFFF_FFFF; // change your pattern here
```



Report (Snapshot, at Least One Table)

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
alu_in_reg	Flip-flop	32	Y	N	Y	N	N	N	N
counter_reg	Flip-flop	5	Y	N	Y	N	N	N	N
shreg_reg	Flip-flop	64	Y	N	Y	N	N	N	N
state_reg	Flip-flop	2	Y	N	Y	N	N	N	N

- ◆ All sequential elements must be **flip-flops**
- ◆ Check by Design Compiler
- ◆ Command:
 - ◆ \$ dv -no_gui
 - ◆ design_vision> read_verilog HW2.v
- ◆ Exit:
 - ◆ design_vision> exit



Submission

- ◆ Deadline: 1 pm on Nov. 28 (Mon.), 2022
 - ◆ No late submission allowed
- ◆ Upload HW2_<student_id>.zip to ceiba
 - ◆ Wrong file or folder format would get 5-point penalty
 - ◆ HW2_<student_id>.zip
 - HW2_<student_id>/
 - HW2_<student_id>/HW2.v
 - HW2_<student_id>/report.pdf
- ◆ Example

```
[r08003@cad29 HW2]$ unzip HW2_r08943003.zip
Archive:  HW2_r08943003.zip
      creating: HW2_r08943003/
      inflating: HW2_r08943003/HW2.v
      extracting: HW2_r08943003/report.pdf
[r08003@cad29 HW2]$ █
```



Score

- ◆ TA will check if your design is reasonable (50 %)
 - ◆ Fits the architecture
 - ◆ Does NOT exist initial block
 - ◆ Does NOT exist delay declaration
 - ◆ Does NOT exist operators including "*" and "/"
 - ◆ **Does NOT exist latches**
 - ◆ **Functionality would only be checked if the demands above are satisfied**
- ◆ `NUM_DATA and `MAX_DELAY will be randomly chosen to check your functionality (50 %)
 - ◆ Default:
`define NUM_DATA 10
`define MAX_DELAY 3